

#Jenny



Finally I get this ebook, thanks for all these I can get now!

#Rio



Cool! I'am really happy

#Markus Jensen



I did not think that this would work, my best friend showed me this website, and it does! I get my most wanted eBook

#Hun Tsu



wtf this great ebook for free?!

#Che Salsa



My friends are so mad that they do not know how I have all the high quality ebook which they do not!

#Diego Butler



so many fake sites. this is the first one which worked! Many thanks

8 Basic Electronics

CONVENTIONAL PROBLEMS

1. Find the potential of points (C) and (D) in Fig. 1.15 if C is located at mid-point of the resistor R. What is the direction of current flow through CD? [-8 V; -16 V; C to D]
2. In Fig. 1.16, the grounding point B is located at one third of resistance R from A. Compute the potential of point (C) and (D). What is the p.d. between A and C? What is the direction of flow of conventional current between points A and C? [0; -4 V; 0; -8 V; 12 V; C to A]
3. Find the reading of the milliammeter connected in the circuit of Fig. 1.17. [8.6 mA]
4. Compute the value of resistor R in Fig. 1.18 if power dissipated by it is 9 W. [4 ohm]
5. What would be the voltmeter responses A and B in series with the combination of Fig. 1.19 if each cell has a voltage of 1.5V? [3V]
6. Find the magnitude and direction of current in Fig. 1.20. [2A; From A to B]
7. In the series circuit of Fig. 1.21, compute the voltage to chassis ground of points A, C and D. What is the p.d. between A and C? [10 V; -10 V; -20 V; 20 V]

[Download PDF version of :](#)
Basic Electronics By BI Theraja Solution Manual